

Verilog Tutorial II

310H:

Honors Computer
Organization and
Programming




Outline

- Sequential Logic in Verilog
 - Schematic Example
 - Verilog
- Delay Modeling in Verilog
 - Assignment Delay
 - Hold and setup time checks
- Tristate Buffers and Busses in Verilog
 - Schematic Example
 - Verilog

Sequential Logic

- Uses a clock to synchronize logic
- Allows for preservation of state over time
 - “Storage” of data
 - Feed back of current state to determine next state
- Allows problems to be broken into discrete steps which can be pipelined

Schematic of Sequential logic

 

Verilog for sequential logic

```
seq1 ( Out, A, B, C, enable, CLK ) ;
    input  A, B, C, enable, CLK;
    output Out;
    wire   pre_out, net0, net1, A_bar;

    invt iv0 (.out (A_bar), .in(A));

    nand2 na0 (.out (net0), .in0 (A), .in1 (B));

    nand2 na1 (.out (net1), .in0 (A_bar), .in1 (C));

    nand2 na3 (.out (pre_out), .in0 (A), .in1 (B));

    dff mydff (.q (Out), .d (pre_out), .en(enable), .clk(CLK));

endmodule
```

D-Flip Flop (Behavioral)

```
module dff ( q, d, clk, en );
    input  d, clk, en;
    output q;
    reg    q;


    always @ ( posedge clk ) begin
        if (en) begin
            q = d;
        end
    end

endmodule // dff
```

Delay Modeling in Verilog

- Verilog allows for path based delay modeling
- Verilog has constructs to check setup and hold time.
- Can be used to ensure signals are available when the clock rises.
- Reasonable results for “first-pass” timing.

Timing example

 

Adding delay to Combinatorial logic

```
module nand2 (out, in0, in1) ;
    input  in0, in1;
    output out;
    assign #1 out = ~(in0 & in1);
endmodule // and2
```

```
module invt (out, in) ;
    input  in;
    output out;
    assign #1 out = ~(in);
endmodule
```

Evaluating setup and hold time for Sequential Logic

```
module dff (q, d, clk, en ) ;
    input  d, clk, en;
    output q;
    reg    q;


    always @ ( posedge clk ) begin
        if (en) begin
            q = d;
        end
    end

    specify
        $setup( d, posedge clk, 1);
        $hold( d, posedge clk, 1);
    endspecify
endmodule // dff
```

Tristate drivers and Busses

- Allow multiple drivers onto one bus as long as the control lines are mutex (mutually exclusive)
- Can act like an implied mux
- When not driven bus will “float” to a Z value.

Tristate Bus w/ drivers and receiver

 

Four bit tristate bus verilog

```
module tri_state ( q, A, B, controll1, control2, enable, clk ) ;
    input  [3:0] A, B;
    input  controll1, control2, enable, clk;
    output [3:0] q;
    tri [3:0]      tri_bus;

    tribuf driverA[3:0] (.out(tri_bus), .in(A), .control(controll1));

    tribuf driverB[3:0] (.out(tri_bus), .in(B), .control(control2));

    dff mydff[3:0] (.q (q), .d (tri_bus), .en(enable), .clk(clk));

endmodule // tri_state
```

Behavioral Verilog for tristate buffer

```
module tribuf ( out, in, control ) ;  
    input  in, control;  
    output out;  
  
    assign #2 out = control ? in : 1'bz;  
  
endmodule // tribuf
```