

Transistor-Level Circuit Analysis

Sol Swords

Talk Outline

- ◆ Motivation
- ◆ What's a transistor? (optional)
- ◆ Bryant's MOSSIM model
- ◆ Demo
- ◆ Improving the tool and the model


Why transistor-level verification

- ♦ rather than gate-level?
 - ♦ Much logic is designed at the gate level or higher, using well-tested standard cells
 - ♦ But custom logic, arrays, ... are designed at the transistor level, not the gate level
 - ♦ Opens possibility of verifying a third-party artifact without access to higher-level representation
 - ♦ Very hard.
 - ♦ Not a focus of this talk.

Why transistor-level verification

- ◆ rather than analog level?
 - ◆ Spice-based analog simulators are used to resolve tricky timing issues, characterize gates, check power usage
 - ◆ But gives much more information than necessary for functional correctness – just need Boolean outputs, not continuous voltages
 - ◆ Transistor-level is faster – can handle much larger designs and longer simulations
 - ◆ Symbolic simulation impractical at analog level

What's a transistor?

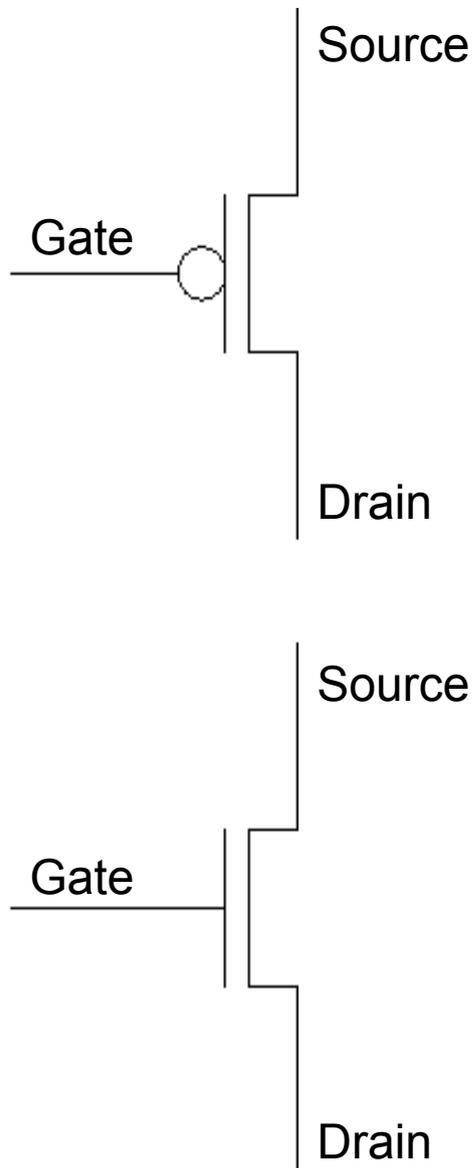

PMOS transistor:

- Gate low: connects source/drain
- Gate high: disconnects source/drain


For our purposes:

Three-terminal electronic component modeled as a voltage-controlled switch.


NMOS transistor:

- Gate high: connects source/drain
- Gate low: disconnects source/drain

Simplest Possible Digital Circuit

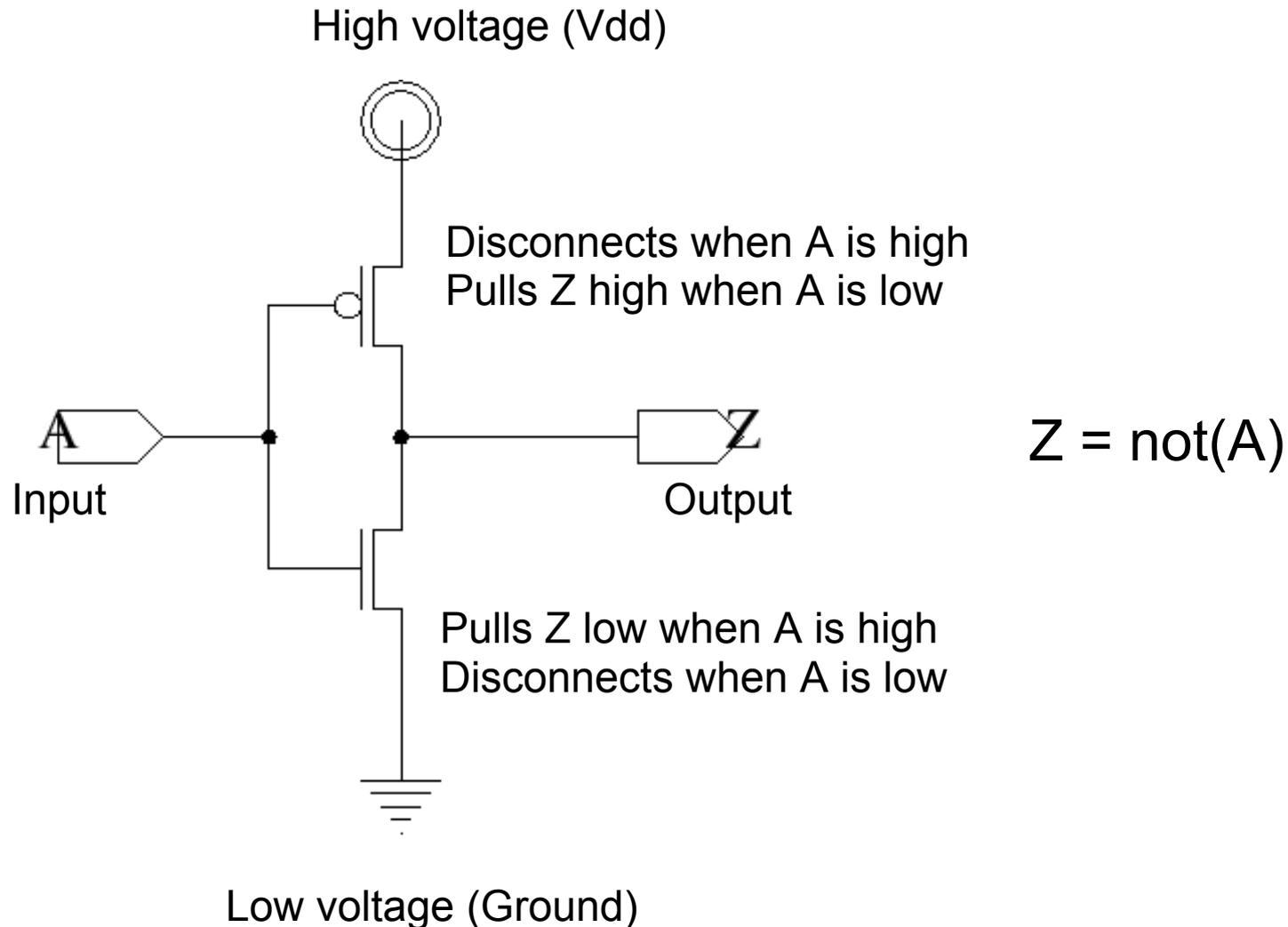



Transistor Strengths

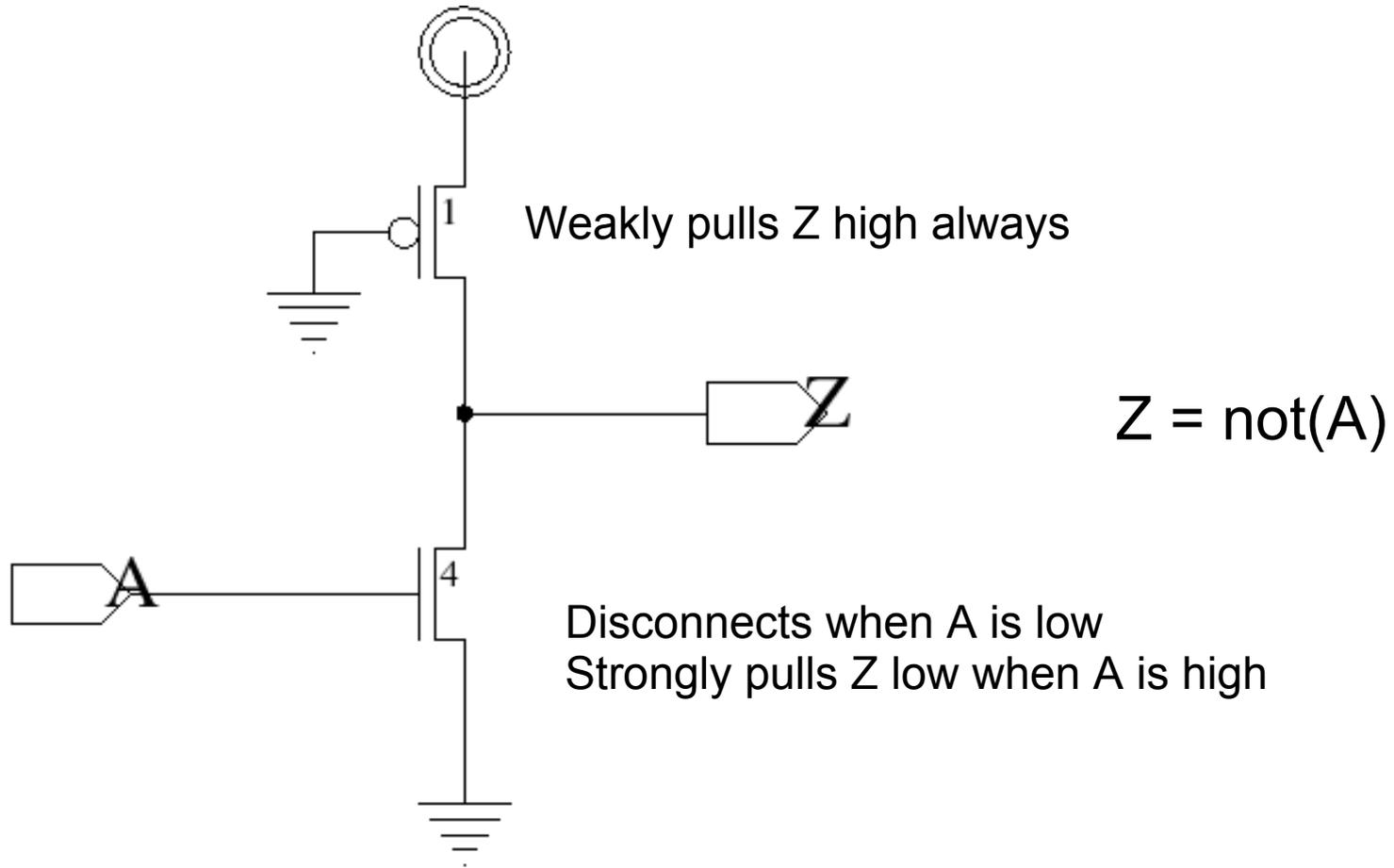

Pseudo-nMOS style – no longer widely used, but illustrative.


Model: Graph representation

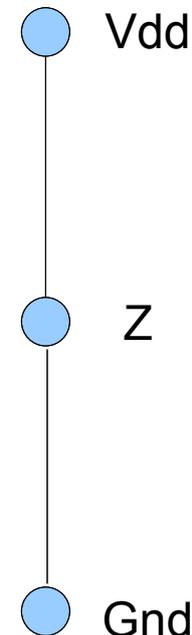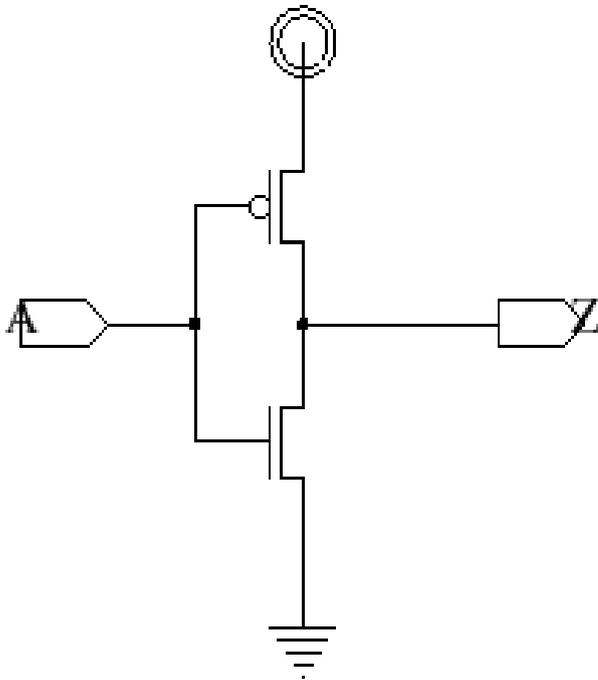- ◆ Circuits are represented as undirected graphs:
 - ◆ Each wire and voltage supply is a vertex
 - ◆ Each transistor source-drain channel is an edge.
 - ◆ Why? Current can flow between source/drain.



Charging Paths

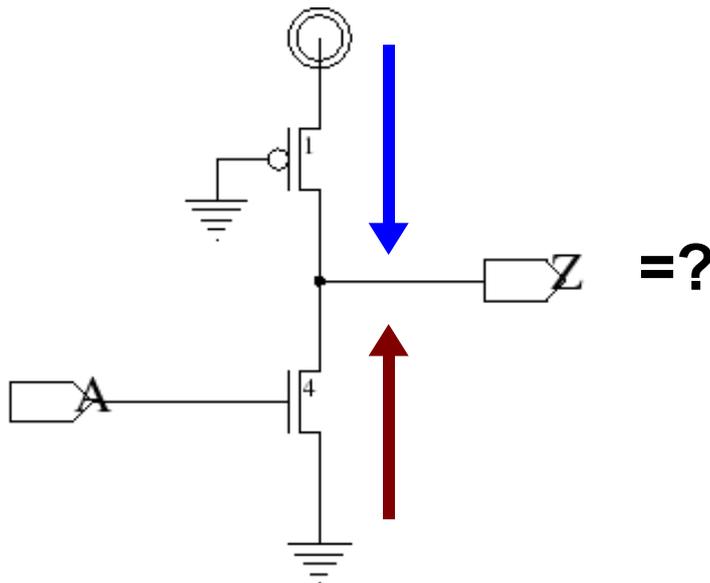
- A wire can be charged or discharged through a path of transistors.
- A path is only active if each transistor in the path is on (gate is high for N, low for P.)
- Multiple active paths may go to a single node – which one sets the node's value?



- May cancel each other and pull to an intermediate voltage
- But don't always – i.e., pseudo-nMOS
- “Comparably strong” paths cancel, or “much stronger” wins


Sharing Charge

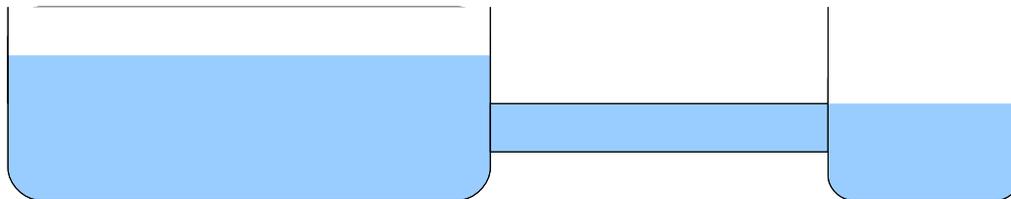- A wire need not be connected to one supply or the other – may float or be connected only to other non-supply wires.
- Wires (nodes) share charge with each other when connected by a path of active transistors.
- Charge flows over connected region until it converges to a uniform voltage.
- Complication: Some wires hold much more charge than others.
- A much larger node can overwhelm small nodes.




Hierarchy of Paths

From supply, through strong transistors

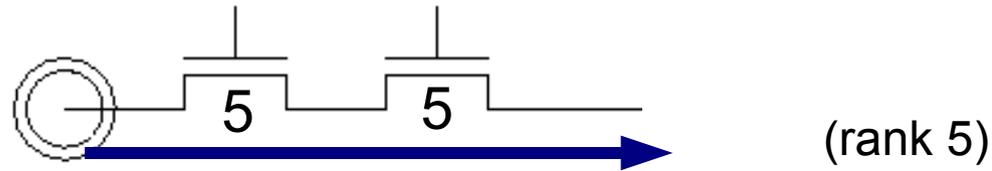


From supply, through weaker transistors

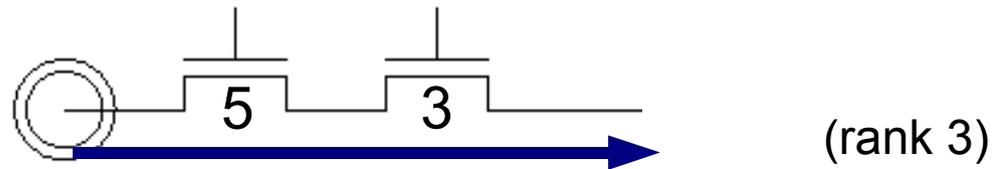


Paths from supply nodes

Paths from non-supply nodes

From large wire

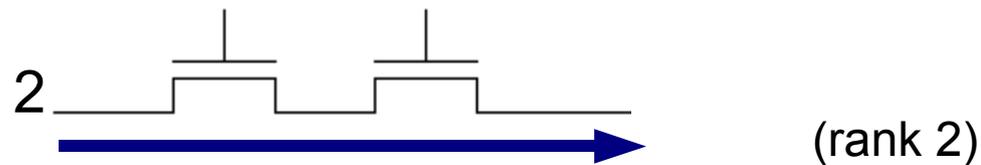


From small wire

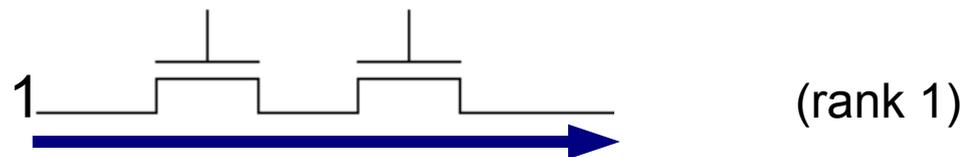

Digression on three-valued logic

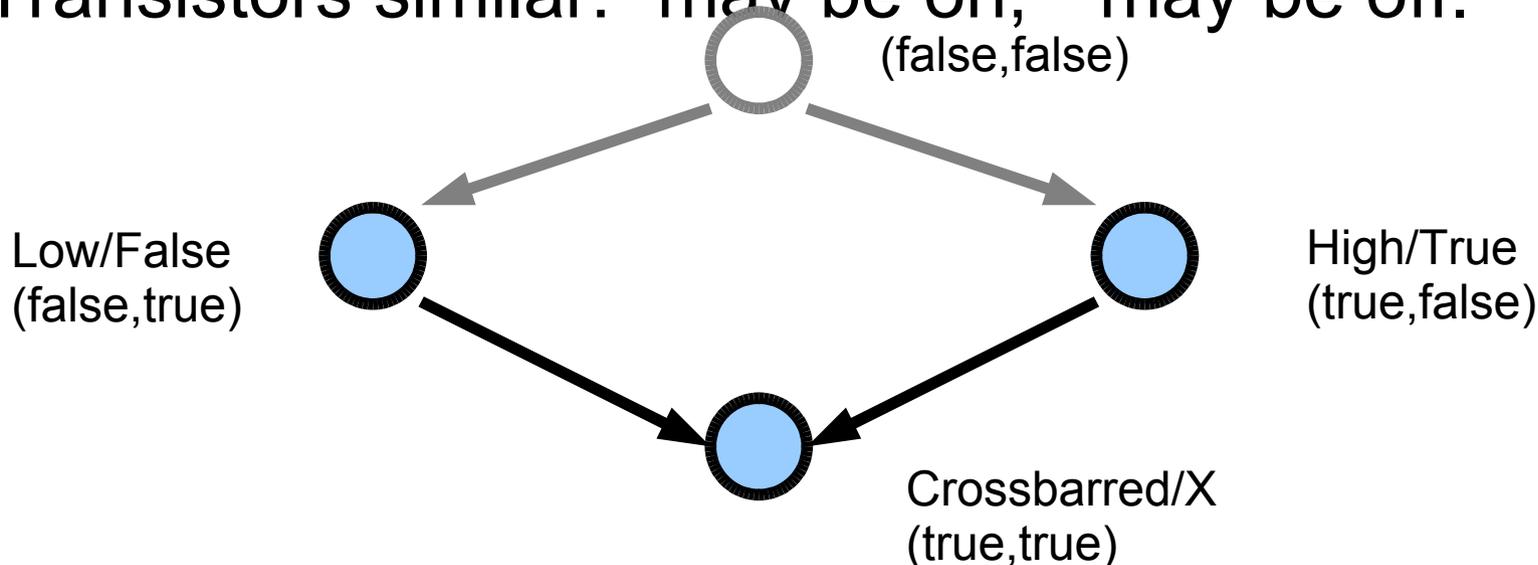- ◆ Need more possibilities than just high/low, true/false
- ◆ Wires can settle to intermediate voltages when paths of comparable strengths fight.
- ◆ Use a lattice model:
 - ◆ represent values by onset-offset pairs: “may be high,” “may be low”
- ◆ Transistors similar: “may be on,” “may be off.”



Final model

For each non-supply node n , find the set of highest-ranked paths to n with all transistors on. If all such paths begin at nodes in the same state, then n gets that state, otherwise X .

- Every node has a path to it: at minimum, the path $n \rightarrow n$ through no transistors.
- New configuration as a function of the initial configuration can be calculated symbolically.
- Is a transistor on or off when its gate is X ?
 - On, to be conservative.

Implementation Details

Definitions:

- ♦ *Possible path*: one where all transistors may be on
 - ♦ “may be on” for a P transistor: gate is low or X
 - ♦ Meaning: The path may set the state of its end node.
 - ♦ *Possible high path*: possible path beginning at a node with onset true.
 - ♦ *Possible low path*: possible path beginning at a node with offset true.
- ♦ *Definite path*: one where no transistors may be off
 - ♦ (“may be off” for a P transistor: gate is high or X)
 - ♦ The path definitely sets the state of its end node.

Implementation Details

- ♦ Iterate down through all possible path ranks. For each node n , update three Boolean symbolic values, considering only paths of the current rank:
 - ♦ n_c (settable) – n may be set by a lower-ranking path.
 - ♦ Starting value: true
 - ♦ New $n_c = n_c \wedge \neg(\text{exists definite path to } n)$
 - ♦ n_1 (onset) – n may be pulled to high voltage.
 - ♦ Starting value: false
 - ♦ New $n_1 = n_1 \vee (n_c \wedge (\text{exists possible high path to } n))$
 - ♦ n_0 (offset) – n may be pulled to low voltage.
 - ♦ Starting value: false
 - ♦ New $n_0 = n_0 \vee (n_c \wedge (\text{exists possible low path to } n))$

Calculating $n_{c,1,0}$

- ◆ Number of paths may be exponential in number of vertices
- ◆ Polynomial algorithm: Gaussian elimination
- ◆ Worst case – $O(v^3)$ BDD operations
- ◆ Typical case – linearly many BDD operations
- ◆ (Still exponential time if BDDs are bad.)

Symbolic Simulation

- ♦ Analysis described so far determines what we do in one symbolic simulation step.
- ♦ Current implementation:
 - ♦ Unit delay timing model
 - ♦ Flatten hierarchical circuits, no shared structure (representation size proportional to circuit size)
 - ♦ Start with most nodes set to X, inputs set to a Boolean constant or variable
 - ♦ At each step, update nodes affected by last step.
- ♦ Demo

Planned Improvements

- ◆ Hierarchy
 - ◆ Circuits are designed in reusable blocks; they should be analyzed that way as well
- ◆ Stored charge is only important on certain nodes
 - ◆ Smaller processes have more leakage, so nodes don't stay floating for long
 - ◆ (Conservatively) ignoring stored charge allows a large speedup; affects correctness in rare cases
 - ◆ Possible to recognize dynamic nodes automatically, or require user input?

Planned Improvements

- ◆ Combinational logic elimination
 - ◆ Get outputs as a function of inputs once and for all, then ignore intermediate nodes
 - ◆ Need intermediate nodes if we care about glitching
 - ◆ Requires adjustment to timing
 - ◆ Big logic cloud shouldn't count as a single gate delay
- ◆ Timing model improvement
 - ◆ Unit timing may be too inaccurate
 - ◆ Need to allow for wire delays, not just logic
 - ◆ Logical effort? Parse output from timing tools?
User override?

Theorems about transistors

- ♦ Analyzer and simulator are written in ACL2, logic mode.
 - ♦ Will I prove them correct?
 - ♦ No.
 - ♦ Within the realm of possibility to prove that the Gaussian elimination algorithm is equivalent to iteration over all paths (for example), but not high priority.
 - ♦ Might be used for theorems about designs, like

```
(equal (eval-bdd (simulator '(...))  
                (list a b c))  
       (spec-function a b c))
```

Bibliography

- ♦ Randal E. Bryant, “Boolean Analysis of MOS Circuits,” *IEEE Transactions on Computer-Aided Design of Integrated Circuits and Systems*, pp. 634-649, July 1987.
- ♦ Randal E. Bryant, “Algorithmic Aspects of Symbolic Switch Network Analysis,” *IEEE Transactions on Computer-Aided Design of Integrated Circuits and Systems*, pp. 618-633, July 1987.

Path strength

- ♦ Rank *charging paths* to storage nodes using node and transistor ranks:

Strength(p) = the minimum of the size of the starting node and the strengths of the transistors in the path.

$$= \text{Min}(\text{size}[\text{startnode}[p]], \text{Min}(\{\text{strength}[d] \mid d \text{ in transistors}[p]\})).$$

Formalizing the model

- ♦ Rank node sizes and transistor strengths:
 - ♦ Supply node size (constant)
 - > transistor strengths
 - > storage node sizes
- ♦ All ranks are integers
- ♦ Ranks have “order of magnitude” semantics
 - ♦ Comparably sized nodes have same rank
 - ♦ Transistors of comparable strength have same rank

Supply nodes

- ♦ Supply nodes hold effectively infinite charge
- ♦ Supply node voltages are unaffected by the modeled circuit
 - ♦ Even if two opposite supply nodes are shorted.
- ♦ A non-supply node can be connected to two opposite supplies – what happens?
 - ♦ Maybe crossbarred (X – bad state)
 - ♦ But maybe not – e.g. pseudo-nMOS.
 - ♦ Path with stronger transistors wins

Implementation Details

- ♦ Iterate down through the path ranks. For each:
 - ♦ Record each node's updated value (onset and offset) as a symbolic formula (BDD) in terms of the previous circuit state. Consider only paths of the current rank.
 - ♦ Record whether each node may still be updated at a lower rank, also as a symbolic formula. True if there were no paths of the current rank or higher.
- ♦ Gaussian elimination algorithm instead of enumeration of all paths
 - ♦ $O(v^3)$ (usually fewer) BDD operations instead of exponentially many.