

Self-Timed Circuits

Ivan Sutherland
Portland State University

ivans@cecs.pdx.edu

Asynchronous Research Center
Portland State University
October 2011

Offering freedom from the tyranny of the clock

Calibration

- This font size appears in the slides
- **If you cannot read the line above, consider moving closer to the screen**

About the ARC at Portland State

- **People**
 - > Marly Roncken (ex Philips & Intel) now PSU – CS Dept.
 - > Ivan Sutherland (ex Sun) now PSU – ECE Dept.
 - > Willem Mallon (ex Philips & NXP) now PSU – CS Dept.
- **Sponsorship**
 - > College of Engineering, PSU
 - > Oracle
 - > DARPA
 - > Seeking additional sponsors

Outline

- Kinetic Learning Activity (KLA)
- Pipelines
- Control protocols
- Performance & Logical Effort
- Data formats
- Gate models
 - > semi modular versus inertial delay

KLA rules

- Predecessor and successor
- Use only one hand
- Pred has object AND you don't
- Take from predecessor
- NEVER PUT to successor

Pipeline action

- Conditions for action
 - > predecessor proffers data
 - > successor has space
- Three part atomic action:
 - > copy data
 - > make successor FULL
 - > make predecessor EMPTY

Pipeline is:

- Logic stage “L”
- Wires “w”

- w L w L w L w L w L w L w

- Wires may hold data (or not)

Control protocols

- Single wire (GasP)
 - > HI = data valid = FULL
- Two wires – four phase
 - > request HI = data valid
 - > acknowledge HI = data accepted
- Two wires – two phase NRZ
 - > differ = data valid = FULL
 - > double data rate (DDR)


6-4 GasP circuit

- Single control wire plus data
 - > HI is FULL convention
 - > bundled data
 - > control wire is bidirectional
- Least logical effort => fastest
 - > forward latency = 6
 - > reverse latency = 4
- Normally opaque data latches

October 30, 2011

Slide 9

GasP circuit diagram

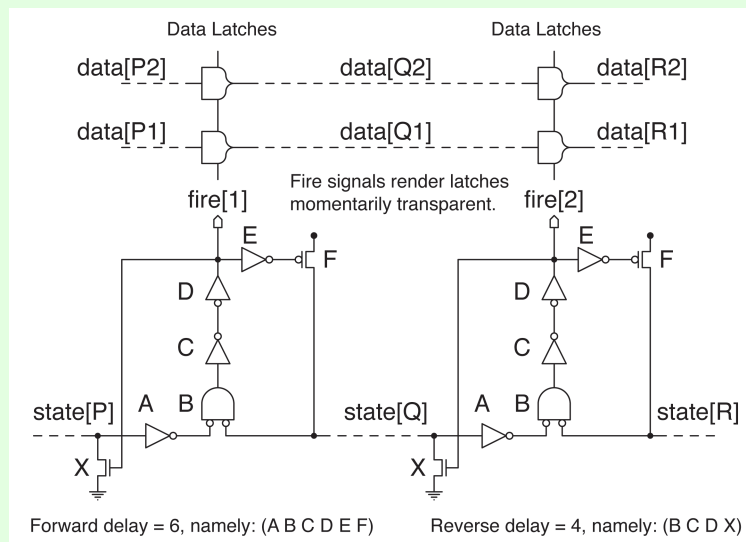

October 30, 2011

Slide 10


Charlie box

- Two wires between stages
 - > differ = FULL
 - > bundled data
 - > acknowledge after capture
- Fast in forward direction
 - > forward = 2 via one latch
 - > reverse = 4 via XOR + latch
- Normally transparent data latches

October 30, 2011

Slide 11

Charlie box circuit diagram

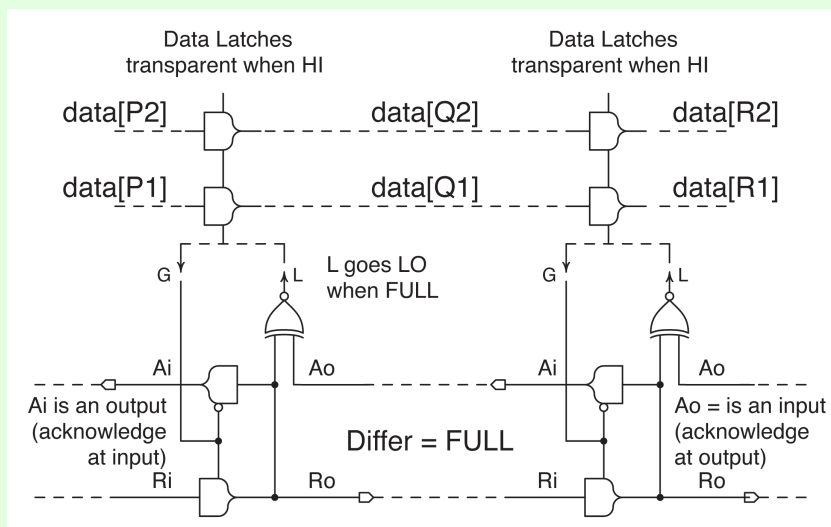

October 30, 2011

Slide 12

Pipeline essentials

- One AND function
 - > pred FULL *and* succ EMPTY
- Data captured in latches or flip flops
- Some relative timing assumptions

- Compare with source clocking

Source and sink clocking

- Source clocking
 - > clock moves forward with data

- Sink clocking
 - > clock moves back with space


Canopy graph

- Throughput versus occupancy
 - > throughput in items/time: GDI/s
 - > occupancy in items/length
- Maximum throughput
- Elastic = variable occupancy
 - > can insert if not full
 - > can withdraw if not empty

October 30, 2011

Slide 15

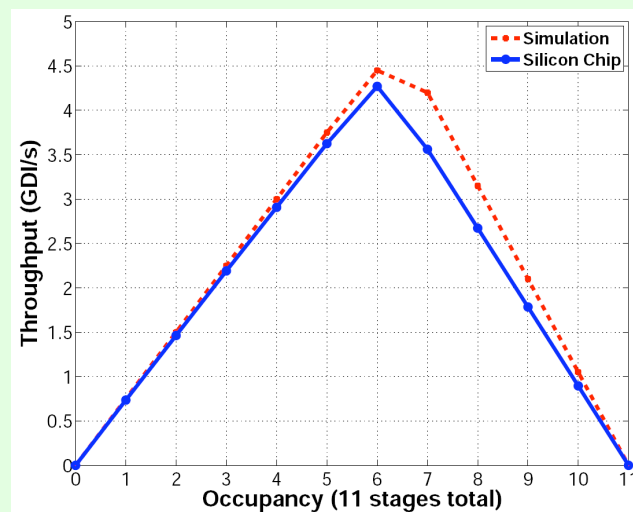Throughput vs Occupancy for ring of 11 stages




October 30, 2011



Slide 16

Infinity test


Demand Merge

 

Data-directed Branch

  

Infinity: Throughput vs Occupancy

 


Mutual exclusion

- Two events at “same” time
 - > which choice doesn't matter
 - > but choice must be clean
- Flip flop can hang metastable
 - > exit is Poisson distributed
 - > may take a long time, but rarely will
- Asynchronous system can wait

Continental divide



Mutual exclusion (Seitz)

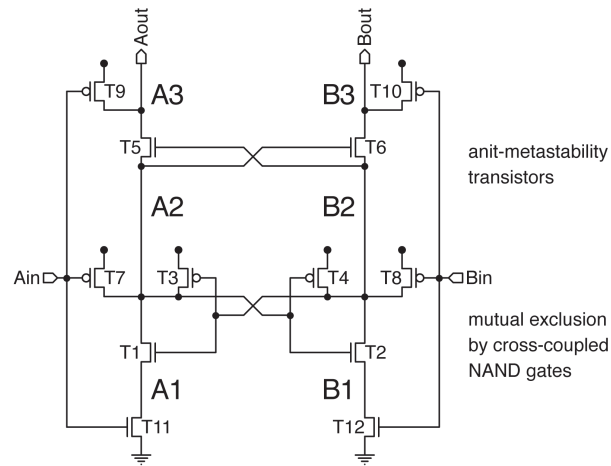

October 30, 2011

Slide 21

Blend control with data

- Two wires per bit (like domino)
 - > LO + LO = invalid
 - > LO + HI = one
 - > HI + LO = zero
- Plus one acknowledge wire
 - > four-phase, NRZ, or single track
 - > Fulcrum – four phase 18 FO4 cycle

October 30, 2011

Slide 22

Validation issues

- Loops in each pipeline stage
 - > interlocked with AND functions
 - > may not have latches or flip flops
 - > hard to verify with conventional tools
- Slope and delay model
 - > slope converges quickly
 - > delay converges if slope is known
 - > not available in conventional tools

Global state

- Is an unnecessary fiction
- Handshakes isolate local actions
- Transactions are what matters
- Pipelines are easy to think about
 - > local transactions tell all
 - > avoid state explosion
 - > painless concurrency

Fork and join pipes

- Fork sends same data both ways
- Join combines two data inputs
- Fork and join parallel pipelines
 - > storage capacity of the shorter
 - > latency of the slower
 - > *slack matching* avoids
 - excess storage
 - excess latency

Unique verification tasks

- Combinational Loops
- Slack matching
- Working with local state
- Deadlock
 - > wormhole networks OK if no loops
 - > other cases?

Discussion