

CS429: Computer Organization and Architecture

Datapath II

Dr. Bill Young
Department of Computer Science
University of Texas at Austin

Last updated: July 11, 2019 at 09:09

The ISA

Byte	0	1	2	3	4	5	6	7	8	9
halt	0	0								
nop	1	0								
cmovXX rA,rB	2	fn	rA	rB						
irmovq V,rB	3	0	F	rB					V	
rmmovq rA,D(rB)	4	0	rA	rB					D	
mrmmovq D(rB),rA	5	0	rA	rB					D	
OPq rA,rB	6	fn	rA	rB						
jXX Dest	7	fn							Dest	
call Dest	8	0							Dest	
ret	9	0								
pushq rA	A	0	rA	F						
popq rA	B	0	rA	F						

CS429 Slideset 13: 1


Datapath II

CS429 Slideset 13: 2

Datapath II

SEQ Stages

 
- Fetch:** Read instruction from instruction memory.
- Decode:** Read program registers
- Execute:** Compute value or address
- Memory:** Read or write back data.
- Write Back:** Write program registers.
- PC:** Update the program counter.



Fetch Logic

Predefined Blocks

 - PC:** Register containing the PC.
- Instruction memory:** Read 10 bytes (PC to PC+9).
- Split:** Divide instruction byte into icode and ifun.
- Align:** Get fields for rA, rB, and valC.



CS429 Slideset 13: 3


Datapath II

CS429 Slideset 13: 4

Datapath II

Control Logic

 - **Instr. Valid:** Is this instruction valid?
- **Needs regids:** Does this instruction have a register byte?
- **Need valC:** Does this instruction have a constant word?



We can define how the various signals are computed using our HCL language:

```
bool instr_valid = icode in
  { INOP, IHALT, IRRMOVQ, IIRMOVQ, IRMMOVQ, IMRMVQ,
    IOPQ, IJXX, ICALL, IRET, IPUSHQ, IPOPQ };
```

```
bool need_regids =
  icode in { IRRMOVQ, IOPQ, IPUSHQ, IPOPQ,
    IIRMOVQ, IRMMOVQ, IMRMVQ };
```


Decode Logic

Register File

- Read ports A, B
- Write ports E, M
- Addresses are register IDs or 0xF (no access)

Control Logic

 - srA, srB: read port addresses
- dstA, dstB: write port addresses



Note that wires in the implementation have different semantics depending on the operation.

Source A

Where is register A coming from?

	OPq rA,rB	
Decode	valA ← R[rA]	Read operand A
	rmmovq rA,D(rB)	
Decode	valA ← R[rA]	Read operand A
	popq rA	
Decode	valA ← R[%rsp]	Read stack pointer
	jXX Dest	
Decode		No operand
	call Dest	
Decode		No operand
	ret	
Decode	valA ← R[%rsp]	Read stack pointer


```
int srcA = [
  icode in { IRRMOVQ, IRMMOVQ, IOPQ, IPUSHQ }: rA;
  icode in { IPOPQ, IRET }: RESP;
  1: RNONE # Don't need register
];
```

Units

- ALU: Implements the 4 required functions, and generates condition code values.
- CC: Register with 3 condition code bits.
- bcond: computes branch flag.

Control Logic

 - Set CC: should condition code register be loaded?
- ALU A: Input A to ALU
- ALU B: Input B to ALU
- ALU fun: What function should ALU compute?



What is feeding the A input to the ALU?

	OPq rA,rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovq rA,D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popq rA	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -8$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer

```

int aluA = [
    icode in { IRRMOVQ, IOPQ }: valA;
    icode in { IIRMOVQ, IRMMOVQ, IMRMVQ }: valC;
    icode in { ICALL, IPUSHQ }: -8;
    icode in { IRET, IPOPQ }: 8;
    # Other instructions don't need an ALU
];

```

ALU Operation

What function should the ALU perform?

	OPq rA,rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation (op)
	rmmovq rA,D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address (add)
	popq rA	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer (add)
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -8$	Decrement stack pointer (add)
	ret	
Execute	$valE \leftarrow valB + 8$	Increment stack pointer (add)

```

int alufun = [
    icode == IOPQ: ifun;
    1: ALUADD;
];

```


Memory Logic

Memory

- Reads or writes memory word.

Control Logic

 - Mem. read: should word be read?
- Mem. write: should word be written?
- Mem. addr.: select address
- Mem. data: select data



What memory address is stored / loaded?

	OPq rA,rB	
Memory		No operation
	rmmovq rA,D(rB)	
Memory	M8[valE] $\leftarrow$ valA	Write value to memory
	popq rA	
Memory	valM $\leftarrow$ M8[valA]	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	M8[valE] $\leftarrow$ valP	Write return value on stack
	ret	
Memory	valM $\leftarrow$ M8[valA]	Increment stack pointer

```
int mem_addr = [
    icode in { IRMMOVQ, IPUSHQ, ICALL, IMRMVQ } : valE;
    icode in { IPOPQ, IRET } : valA;
    # Other instructions don't need address
];
```

For what instructions is memory read?


	OPq rA,rB	
Memory		No operation
	rmmovq rA,D(rB)	
Memory	M8[valE] $\leftarrow$ valA	Write value to memory
	popq rA	
Memory	valM $\leftarrow$ M8[valA]	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	M8[valE] $\leftarrow$ valP	Write return value on stack
	ret	
Memory	valM $\leftarrow$ M8[valA]	Increment stack pointer

```
bool mem_read = icode in { IMRMVQ, IPOPQ, IRET };
```

Write Back Logic

Notice for Write-back, there is no explicit hardware here.

 That's because the location for writing back was determined at the decode stage. At this stage we have simply computed the values to write-back into the register file!



Destination E

Where to store the value computed by the ALU?

	OPq rA,rB	
Write-back	R[rB] $\leftarrow$ valE	Write back result
	rmmovq rA,D(rB)	
Write-back		None
	popq rA	
Write-back	R[%rsp] $\leftarrow$ valE	Update stack pointer
	jXX Dest	
Write-back		None
	call Dest	
Write-back	R[%rsp] $\leftarrow$ valE	Update stack pointer
	ret	
Write-back	R[%rsp] $\leftarrow$ valE	Update stack pointer


```
int dstE = [
    icode in { IRRMOVQ, IIRMOVQ, IOPQ } : rB;
    icode in { IPUSHQ, IPOPQ, ICALL, IRET } : RESP;
    1: RNONE # Don't need register
];
```

New PC

Select next value of PC.

Depends on:

 - `icode`: current instruction
- `Bch`: result of branch logic
- `valC`: constant from instruction word
- `valM`: value from memory (stack)
- `valP`: predicted value from fetch




What is the new value of the PC?

	OPq rA,rB	
PC update	PC $\leftarrow$ valP	Update PC (by 2)
	rmmovq rA,D(rB)	
PC update	PC $\leftarrow$ valP	Update PC (by 10)
	popq rA	
PC update	PC $\leftarrow$ valP	Update PC (by 2)
	jXX Dest	
PC update	PC $\leftarrow$ Bch ? valC : valP	Update PC (to what?)
	call Dest	
PC update	PC $\leftarrow$ valC	Set PC to destination
	ret	
PC update	PC $\leftarrow$ valM	Set PC to return address

```
int new_pc = [
    icode == ICALL: valC;
    icode == IJXX && Bch: ValC;
    icode == IRET: valM;
    1: valP;
];
```

SEQ Operation

 

State: All updated as the clock rises.

- PC register
- Condition Code register
- Register file



Combinational Logic

- ALU
- Control logic

Sequential Logic


- Instruction memory
- Register file
- Data memory

SEQ Operation 2

  


- state is set according to first `irmovq` instruction
- combinational logic is starting to react to state changes

SEQ Operation 3

 

Cycle 1:	0x000:	irmovq	\$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x006:	irmovq	\$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x00c:	addq	%rdx,%rbx	# %rbx <-- 0x300, CC <-- 000
Cycle 4:	0x00e:	je	dest	# Not taken

 


- state is set according to second `irmovq` instruction
- combinational logic generates results for `addq` instruction


CS429 Slideset 13: 21

Datapath II

SEQ Operation 4

 

Cycle 1:	0x000:	irmovq	\$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x006:	irmovq	\$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x00c:	addq	%rdx,%rbx	# %rbx <-- 0x300, CC <-- 000
Cycle 4:	0x00e:	je	dest	# Not taken

 


- state is set according to `addq` instruction
- combinational logic starting to react to state changes


CS429 Slideset 13: 22

Datapath II

SEQ Operation 5

 

Cycle 1:	0x000:	irmovq	\$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x006:	irmovq	\$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x00c:	addq	%rdx,%rbx	# %rbx <-- 0x300, CC <-- 000
Cycle 4:	0x00e:	je	dest	# Not taken

 

- state is set according to `addq` instruction
- combinational logic generates results for `je` instruction

CS429 Slideset 13: 23

Datapath II

SEQ Summary

Implementation

- Express every instruction as a series of simple steps.
- Follow same general flow for each instruction type.
- Assemble registers, memories, predesigned combinational blocks.
- Connect with control logic.

Limitations

- Too slow to be practical. What is the slowest stage?
- In one cycle, must propagate through instruction memory, register file, ALU, and data memory.
- Would need to run the clock very slowly.
- Hardware units are only active for a fraction of the clock cycle.

CS429 Slideset 13: 24

Datapath II

