


Systems I

Datapath Design II

Topics

- Control flow instructions
- Hardware for sequential machine (SEQ)

Executing Jumps

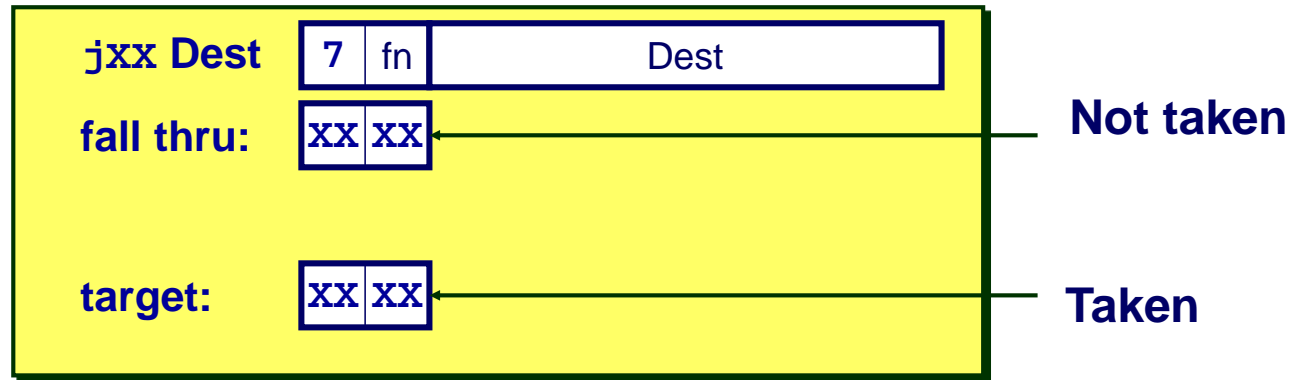

Fetch

- Read 5 bytes
- Increment PC by 5

Decode

- Do nothing

Execute

- Determine whether to take branch based on jump condition and condition codes

Memory

- Do nothing

Write back

- Do nothing

PC Update


- Set PC to `Dest` if branch taken or to incremented PC if not branch

Stage Computation: Jumps

	jXX Dest	
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
	$\text{valC} \leftarrow M_4[\text{PC}+1]$	Read destination address
	$\text{valP} \leftarrow \text{PC}+5$	Fall through address
Decode		
Execute	$\text{Bch} \leftarrow \text{Cond}(\text{CC}, \text{ifun})$	Take branch?
Memory		
Write back		
PC update	$\text{PC} \leftarrow \text{Bch} ? \text{valC} : \text{valP}$	Update PC

- Compute both addresses
- Choose based on setting of condition codes and branch condition

Executing call

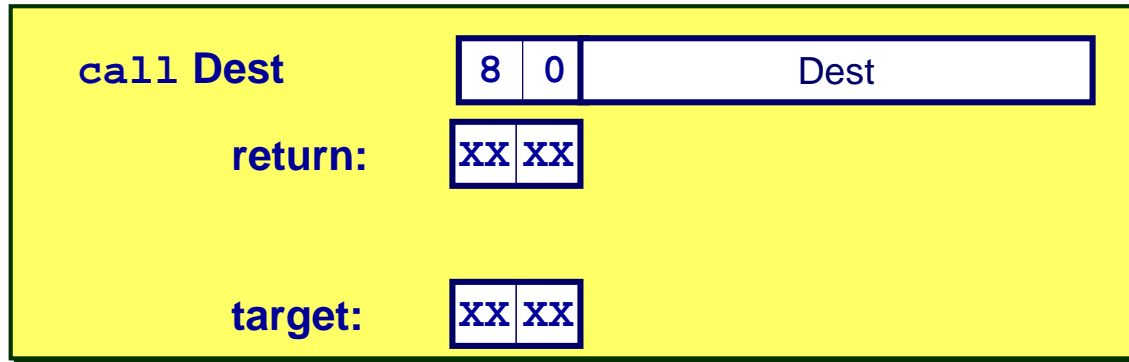

Fetch

- Read 5 bytes
- Increment PC by 5

Decode

- Read stack pointer

Execute

- Decrement stack pointer by 4

Memory

- Write incremented PC to new value of stack pointer

Write back

- Update stack pointer

PC Update


- Set PC to Dest

Stage Computation: call

	call Dest	
Fetch	$icode:ifun \leftarrow M_1[PC]$	Read instruction byte
	$valC \leftarrow M_4[PC+1]$	Read destination address
	$valP \leftarrow PC+5$	Compute return point
Decode	$valB \leftarrow R[\%esp]$	Read stack pointer
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
Memory	$M_4[valE] \leftarrow valP$	Write return value on stack
Write back	$R[\%esp] \leftarrow valE$	Update stack pointer
PC update	$PC \leftarrow valC$	Set PC to destination

- Use ALU to decrement stack pointer
- Store incremented PC

Executing `ret`

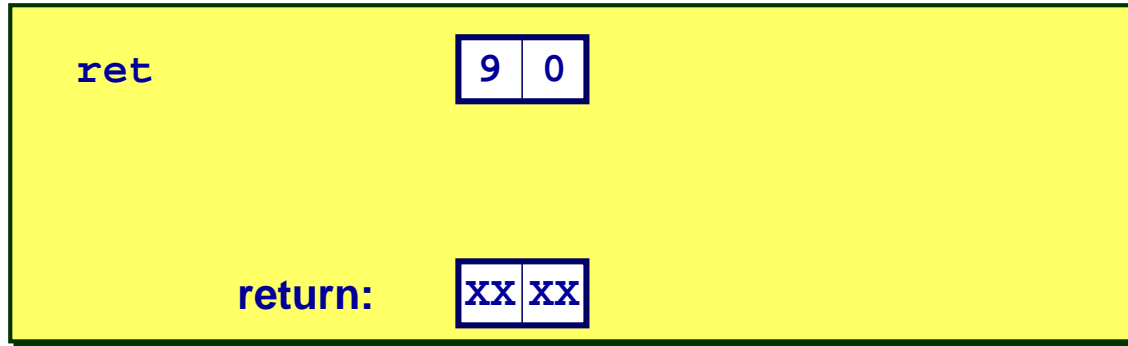

Fetch

- Read 1 byte

Decode

- Read stack pointer

Execute

- Increment stack pointer by 4

Memory

- Read return address from old stack pointer

Write back

- Update stack pointer

PC Update

- Set PC to return address

Stage Computation: ret

ret		
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
Decode	$\text{valA} \leftarrow R[\%esp]$ $\text{valB} \leftarrow R[\%esp]$	Read operand stack pointer Read operand stack pointer
Execute	$\text{valE} \leftarrow \text{valB} + 4$	Increment stack pointer
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address
Write back	$R[\%esp] \leftarrow \text{valE}$	Update stack pointer
PC update	$\text{PC} \leftarrow \text{valM}$	Set PC to return address

- Use ALU to increment stack pointer
- Read return address from memory

Computation Steps

		OPI rA, rB
Fetch	icode,ifun	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$
	rA,rB	$\text{rA:rB} \leftarrow M_1[\text{PC}+1]$
	valC	
	valP	$\text{valP} \leftarrow \text{PC}+2$
Decode	valA, srcA	$\text{valA} \leftarrow R[\text{rA}]$
	valB, srcB	$\text{valB} \leftarrow R[\text{rB}]$
Execute	valE	$\text{valE} \leftarrow \text{valB OP valA}$
	Cond code	Set CC
Memory	valM	
Write back	dstE	$R[\text{rB}] \leftarrow \text{valE}$
	dstM	
PC update	PC	$\text{PC} \leftarrow \text{valP}$

Read instruction byte
 Read register byte
 [Read constant word]
 Compute next PC
 Read operand A
 Read operand B
 Perform ALU operation
 Set condition code register
 [Memory read/write]
 Write back ALU result
 [Write back memory result]
 Update PC

- All instructions follow same general pattern
- Differ in what gets computed on each step

Computation Steps

		call Dest	
Fetch	icode,ifun	$icode:ifun \leftarrow M_1[PC]$ $valC \leftarrow M_4[PC+1]$ $valP \leftarrow PC+5$	Read instruction byte
	rA,rB		[Read register byte]
	valC		Read constant word
	valP		Compute next PC
Decode	valA, srcA	$valB \leftarrow R[\%esp]$	[Read operand A]
	valB, srcB		Read operand B
Execute	valE	$valE \leftarrow valB + -4$	Perform ALU operation
	Cond code		[Set condition code reg.]
Memory	valM	$M_4[valE] \leftarrow valP$	[Memory read/write]
Write back	dstE	$R[\%esp] \leftarrow valE$	[Write back ALU result]
	dstM		Write back memory result
PC update	PC	$PC \leftarrow valC$	Update PC

- All instructions follow same general pattern
- Differ in what gets computed on each step

Computed Values

Fetch

icode	Instruction code
ifun	Instruction function
rA	Instr. Register A
rB	Instr. Register B
valC	Instruction constant
valP	Incremented PC

Decode

srcA	Register ID A
srcB	Register ID B
dstE	Destination Register E
dstM	Destination Register M
valA	Register value A
valB	Register value B

Execute

- **valE** **ALU result**
- **Bch** **Branch flag**


Memory

- **valM** **Value from memory**

SEQ Hardware

Key

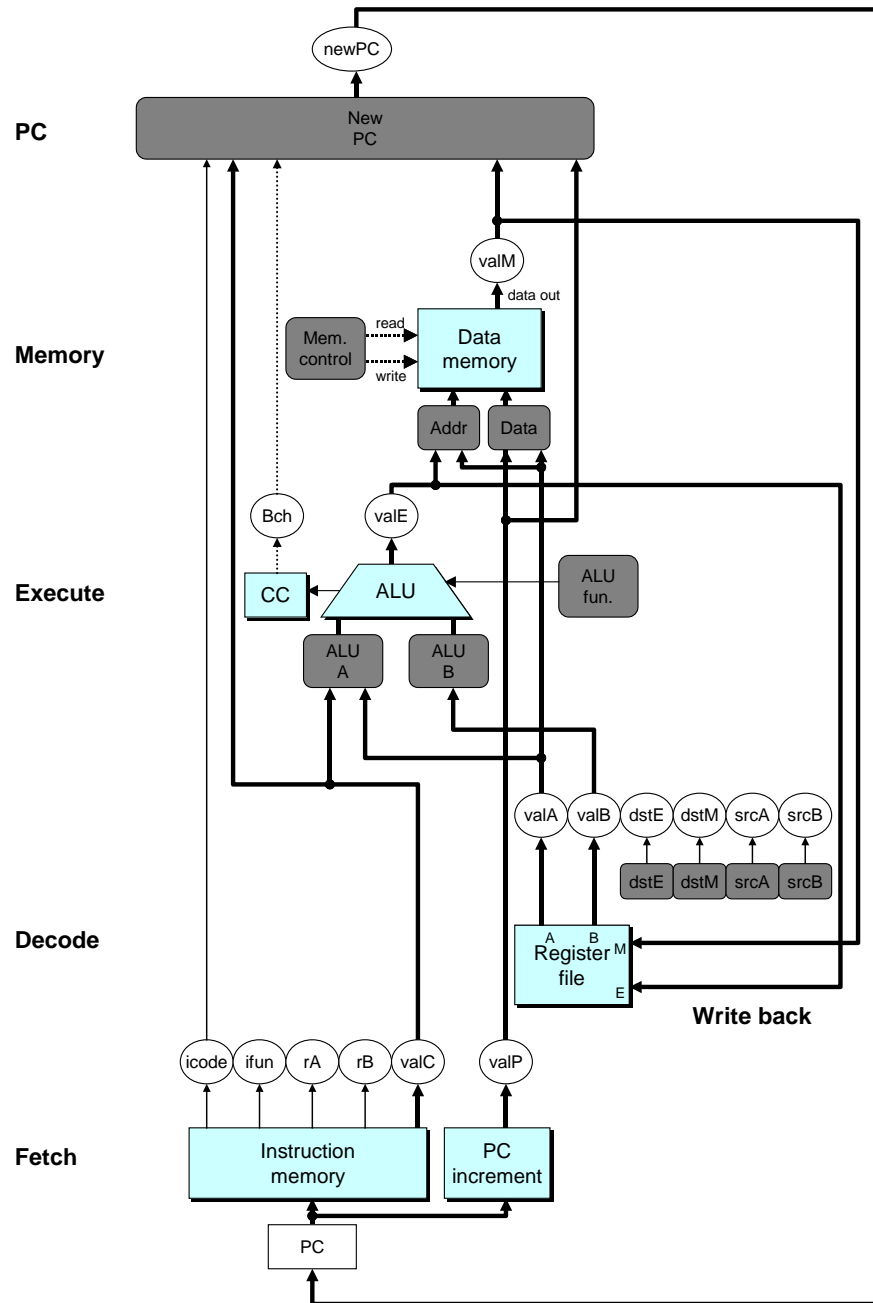- Blue boxes: predesigned hardware blocks
 - E.g., memories, ALU
- Gray boxes: control logic
 - Describe in HCL
- White ovals: labels for signals
- Thick lines: 32-bit word values
- Thin lines: 4-8 bit values
- Dotted lines: 1-bit values



Summary

Today

- Control flow instructions
- Hardware for sequential machine (SEQ)

Next time

- Control logic for instruction execution
- Timing and clocking


Systems I

Datapath Design III

Topics

- Control logic for instruction execution
- Timing and clocking


Fetch Logic

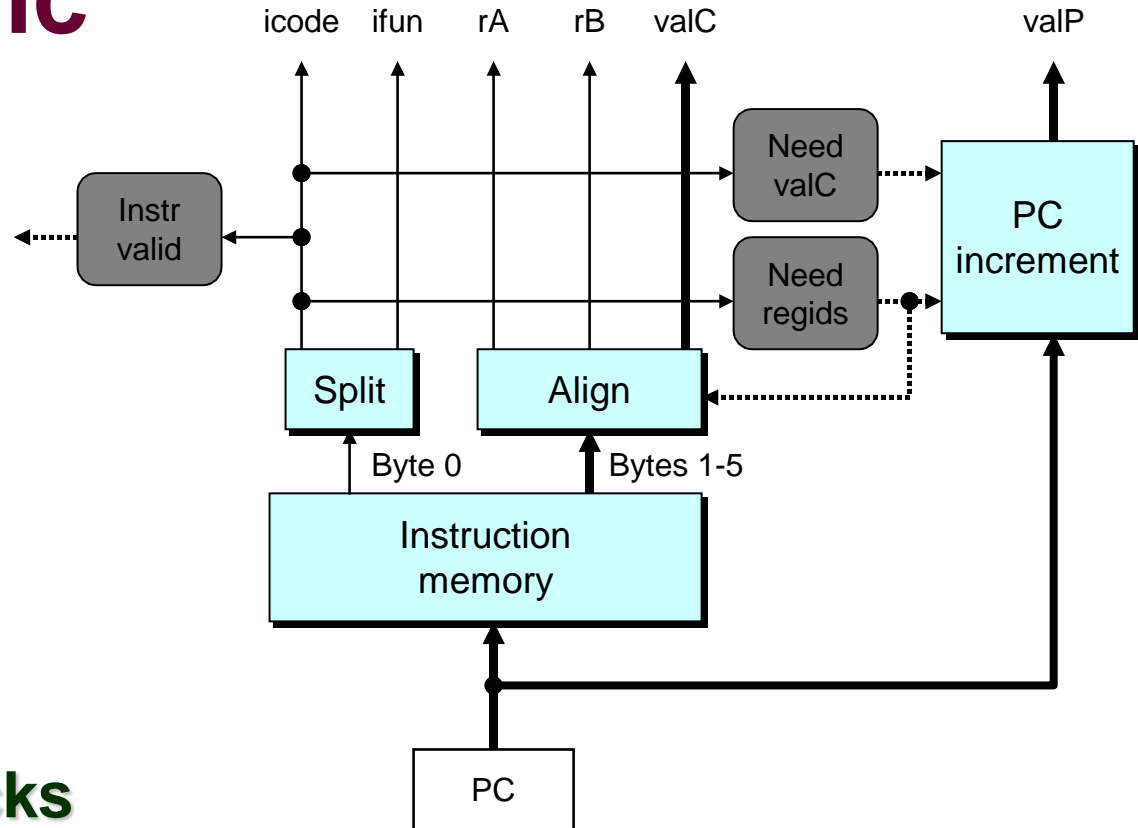

Predefined Blocks

- **PC:** Register containing PC
- **Instruction memory:** Read 6 bytes (PC to PC+5)
- **Split:** Divide instruction byte into icode and ifun
- **Align:** Get fields for rA, rB, and valC

Fetch Logic

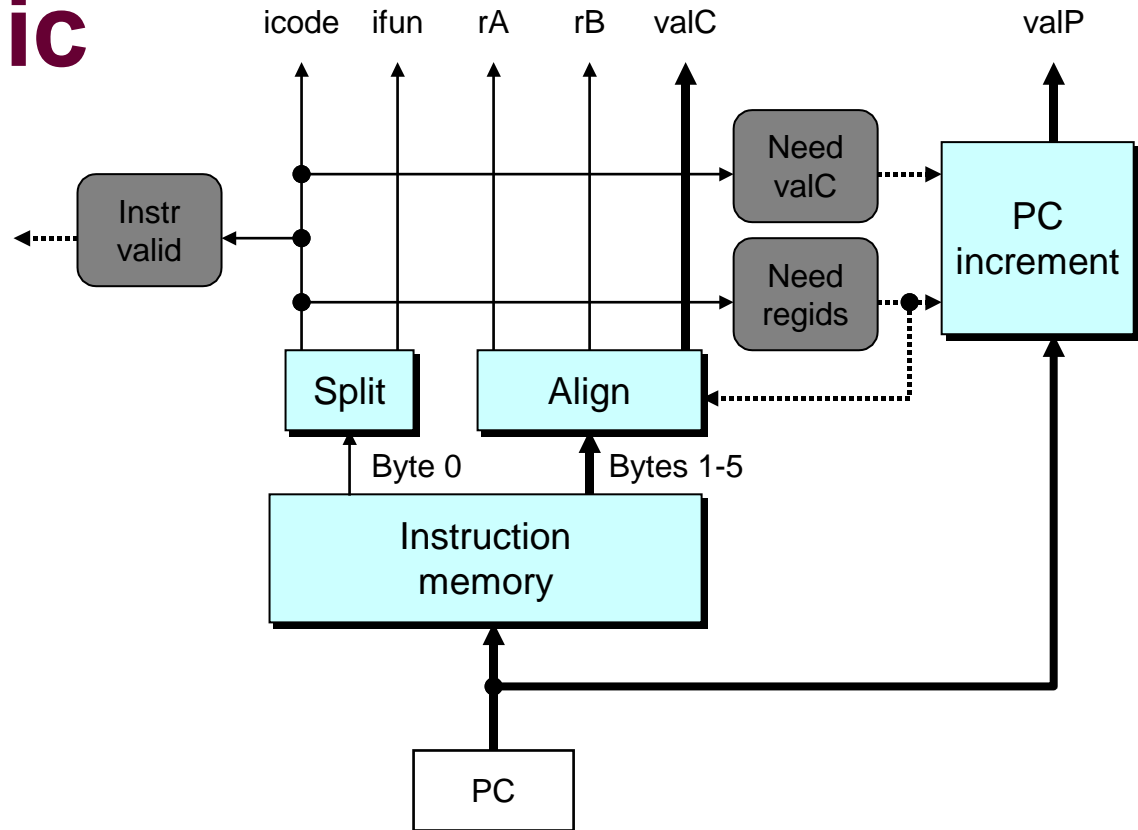


Control Logic

- **Instr. Valid:** Is this instruction valid?
- **Need regids:** Does this instruction have a register byte?
- **Need valC:** Does this instruction have a constant word?


Fetch Control Logic in HCL

```
# Determine instruction code
int icode = [
    imem_error: INOP;
    1: imem_icode;
];
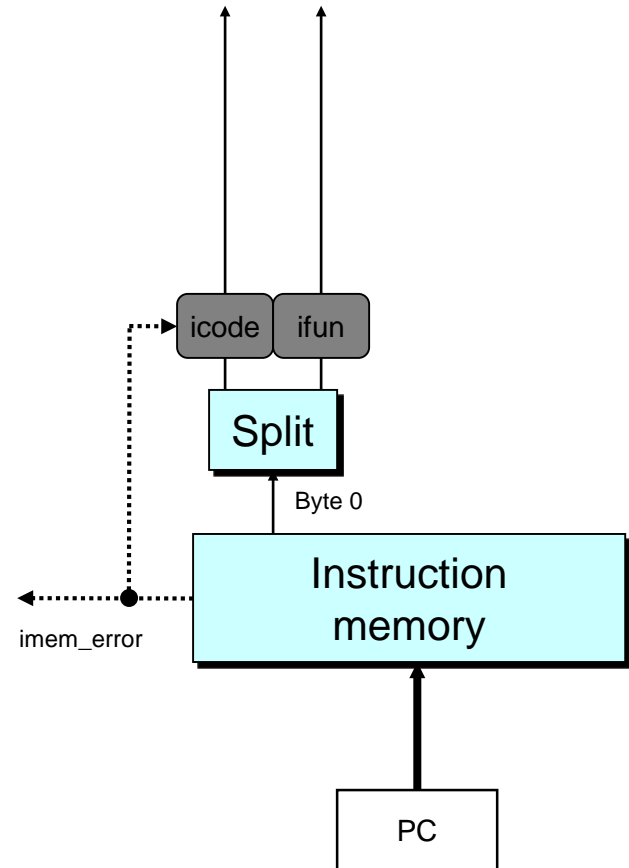
# Determine instruction function
int ifun = [
    imem_error: FNONE;
    1: imem_ifun;
];
```



Fetch Control Logic

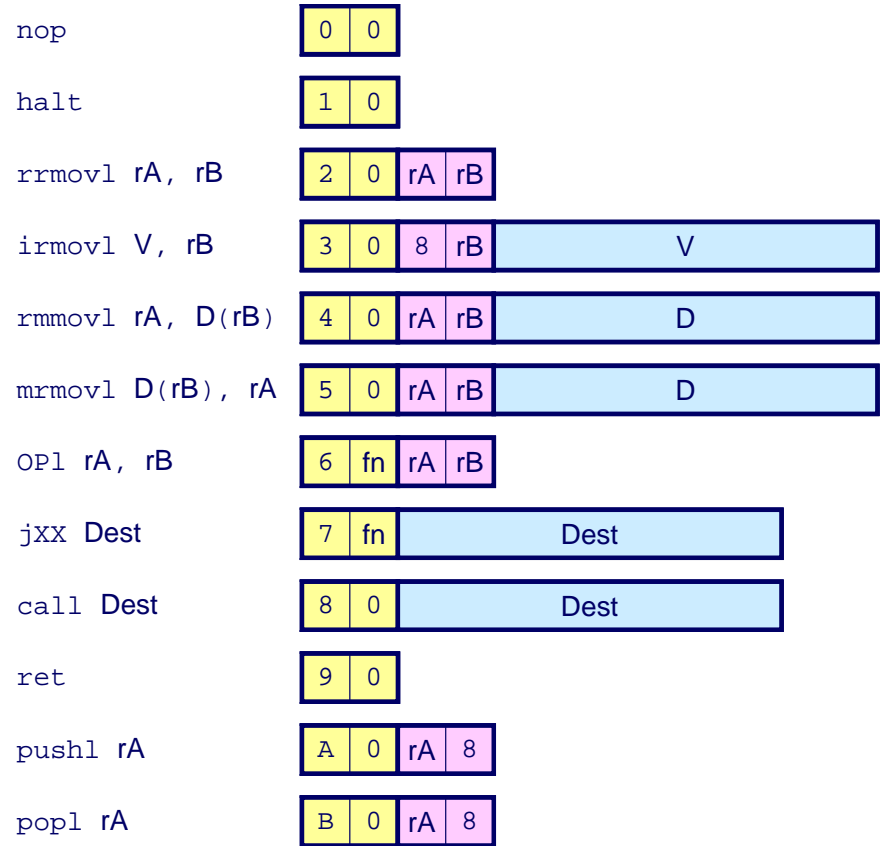

```
bool need_regids =
    icode in { IRRMOVL, IOPL, IPUSHL, IPOPL,
              IIRMOVL, IRMMOVL, IMRMOVL };
```

```
bool instr_valid = icode in
    { INOP, IHALT, IRRMOVL, IIRMOVL, IRMMOVL, IMRMOVL,
      IOPL, IJXX, ICALL, IRET, IPUSHL, IPOPL };
```


Decode Logic

Register File

- Read ports A, B
- Write ports E, M
- Addresses are register IDs or 8 (no access)

Control Logic

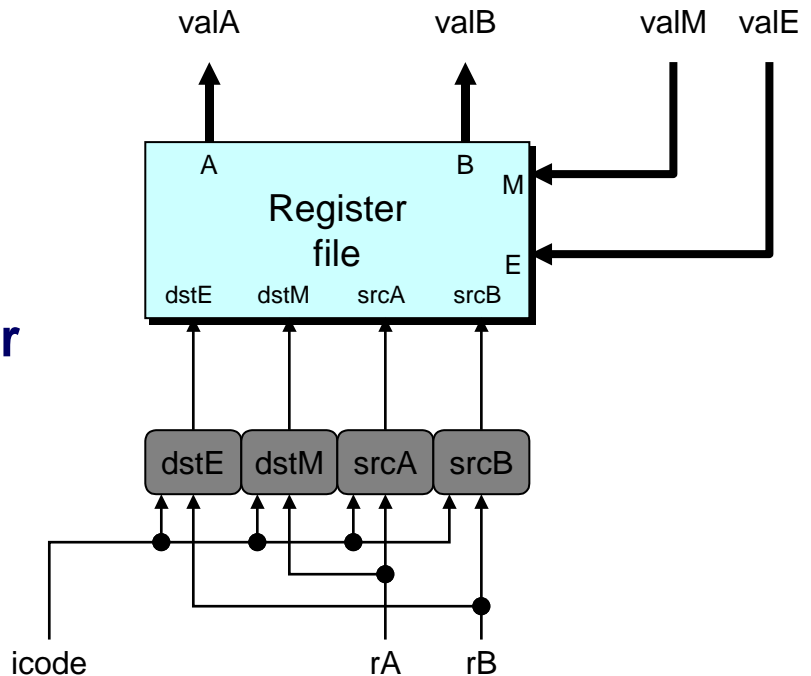- srcA, srcB: read port addresses
- dstA, dstB: write port addresses



A Source

	OPl rA, rB	
Decode	valA ← R[rA]	Read operand A
	rmmovl rA, D(rB)	
Decode	valA ← R[rA]	Read operand A
	popl rA	
Decode	valA ← R[%esp]	Read stack pointer
	jXX Dest	
Decode		No operand
	call Dest	
Decode		No operand
	ret	
Decode	valA ← R[%esp]	Read stack pointer

```
int srcA = [  
    icode in { IRRMOVL, IRMMOVL, IOPL, IPUSHL } : rA;  
    icode in { IPOPL, IRET } : RESP;  
    1 : RNONE; # Don't need register  
];
```

E Destination

	OPl rA, rB	
Write-back	R[rB] ← valE	Write back result
	rmmovl rA, D(rB)	
Write-back		None
	popl rA	
Write-back	R[%esp] ← valE	Update stack pointer
	jXX Dest	
Write-back		None
	call Dest	
Write-back	R[%esp] ← valE	Update stack pointer
	ret	
Write-back	R[%esp] ← valE	Update stack pointer

```
int dstE = [
    icode in { IRRMOVL, IIRMOVL, IOPL } : rB;
    icode in { IPUSHL, IPOPL, ICALL, IRET } : RESP;
    1 : RNONE; # Don't need register
];
```


Execute Logic

Units

- **ALU**
 - Implements 4 required functions
 - Generates condition code values
- **CC**
 - Register with 3 condition code bits
- **bcond**
 - Computes branch flag

Control Logic

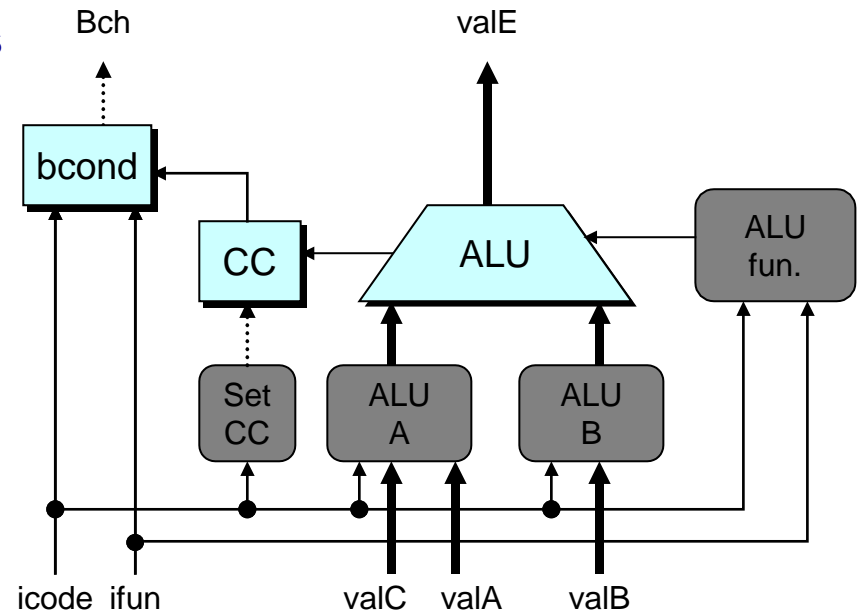- **Set CC:** Should condition code register be loaded?
- **ALU A:** Input A to ALU
- **ALU B:** Input B to ALU
- **ALU fun.:** What function should ALU compute?



ALU A Input

	OPl rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popl rA	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer

```
int aluA = [  
    icode in { IRRMOVL, IOPL } : valA;  
    icode in { IIRMOVL, IRMMOVL, IMRMOVL } : valC;  
    icode in { ICALL, IPUSHL } : -4;  
    icode in { IRET, IPOPL } : 4;  
    # Other instructions don't need ALU  
];
```

ALU Operation

	OPl rA, rB	
Execute	$valE \leftarrow valB \text{ OP } valA$	Perform ALU operation
	rmmovl rA, D(rB)	
Execute	$valE \leftarrow valB + valC$	Compute effective address
	popl rA	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer
	jXX Dest	
Execute		No operation
	call Dest	
Execute	$valE \leftarrow valB + -4$	Decrement stack pointer
	ret	
Execute	$valE \leftarrow valB + 4$	Increment stack pointer

```
int alufun = [  
    icode == IOPL : ifun;  
    1 : ALUADD;  
];
```


Memory Logic

Memory

- Reads or writes memory word

Control Logic

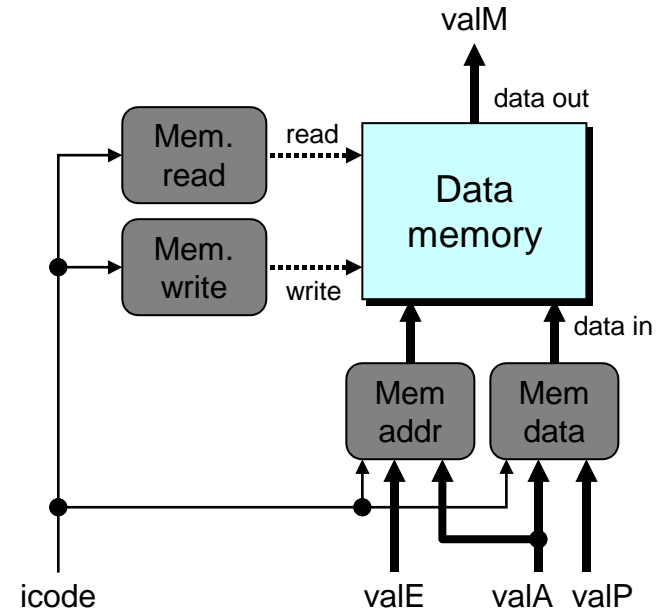
- Mem. read: should word be read?
- Mem. write: should word be written?
- Mem. addr.: Select address
- Mem. data.: Select data



Instruction Status

Control Logic

- **stat**: What is instruction status?

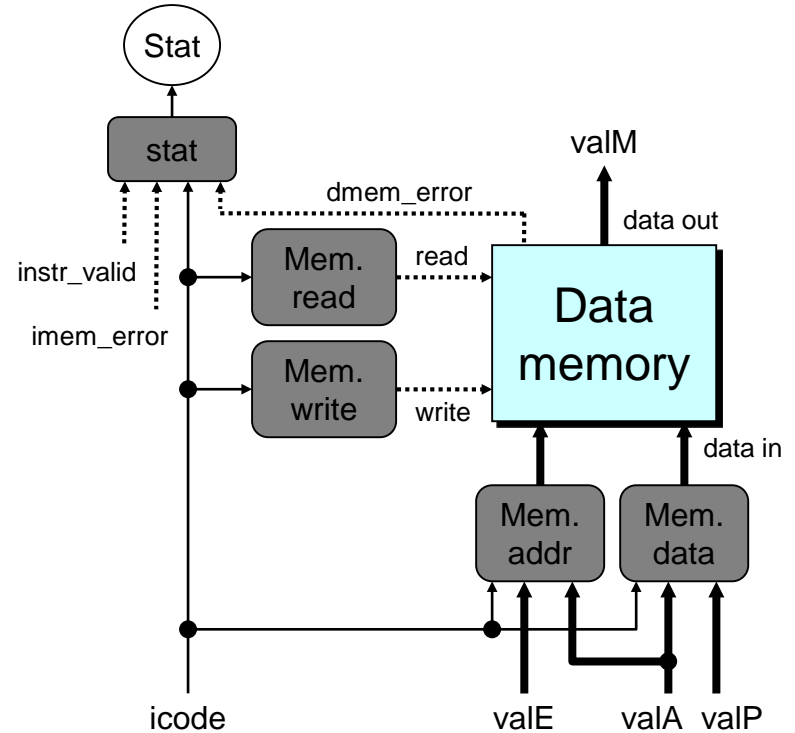

```
## Determine instruction status
int Stat = [
    imem_error || dmem_error : SADR;
    !instr_valid: SINS;
    icode == IHALT : SHLT;
    1 : SAOK;
];
```

Memory Address

	OPl rA, rB	
Memory		No operation
	rmmovl rA, D(rB)	
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
	popl rA	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	$M_4[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
	ret	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address

```
int mem_addr = [  
    icode in { IRMMOVL, IPUSHL, ICALL, IMRMOVL } : valE;  
    icode in { IPOPL, IRET } : valA;  
    # Other instructions don't need address  
];
```

Memory Read


	OPl rA, rB	
Memory		No operation
	rmmovl rA, D(rB)	
Memory	$M_4[\text{valE}] \leftarrow \text{valA}$	Write value to memory
	popl rA	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read from stack
	jXX Dest	
Memory		No operation
	call Dest	
Memory	$M_4[\text{valE}] \leftarrow \text{valP}$	Write return value on stack
	ret	
Memory	$\text{valM} \leftarrow M_4[\text{valA}]$	Read return address

```
bool mem_read = icode in { IMRMOVL, IPOPL, IRET };
```

PC Update Logic

New PC

- Select next value of PC

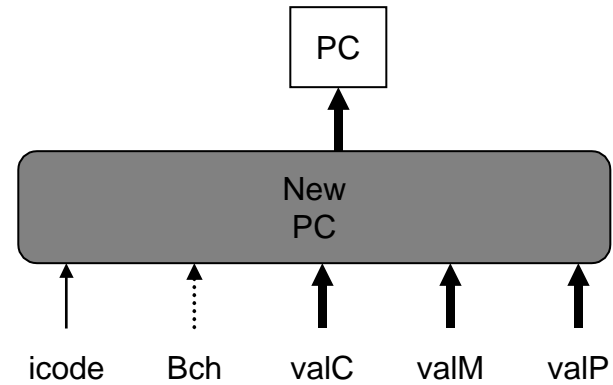


PC Update

	OPl rA, rB	
PC update	PC ← valP	Update PC
	rmmovl rA, D(rB)	
PC update	PC ← valP	Update PC
	popl rA	
PC update	PC ← valP	Update PC
	jXX Dest	
PC update	PC ← Bch ? valC : valP	Update PC
	call Dest	
PC update	PC ← valC	Set PC to destination
	ret	
PC update	PC ← valM	Set PC to return address

```
int new_pc = [  
    icode == ICALL : valC;  
    icode == IJXX && Bch : valC;  
    icode == IRET : valM;  
    1 : valP;  
];
```

SEQ Operation

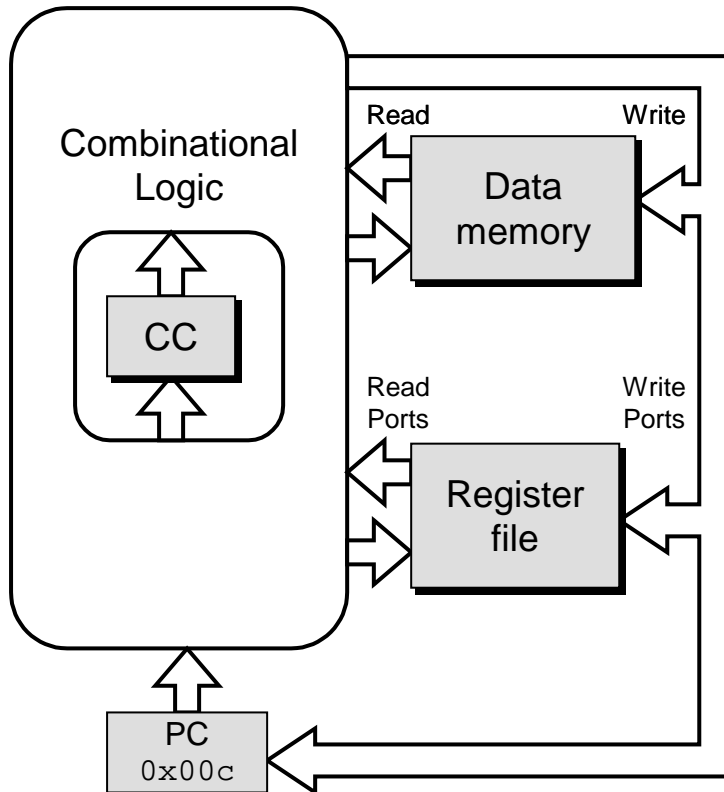

State



- PC register
- Cond. Code register
- Data memory
- Register file

All updated as clock rises

Combinational Logic



- ALU
- Control logic
- Memory reads
 - Instruction memory
 - Register file
 - Data memory

SEQ Operation #2

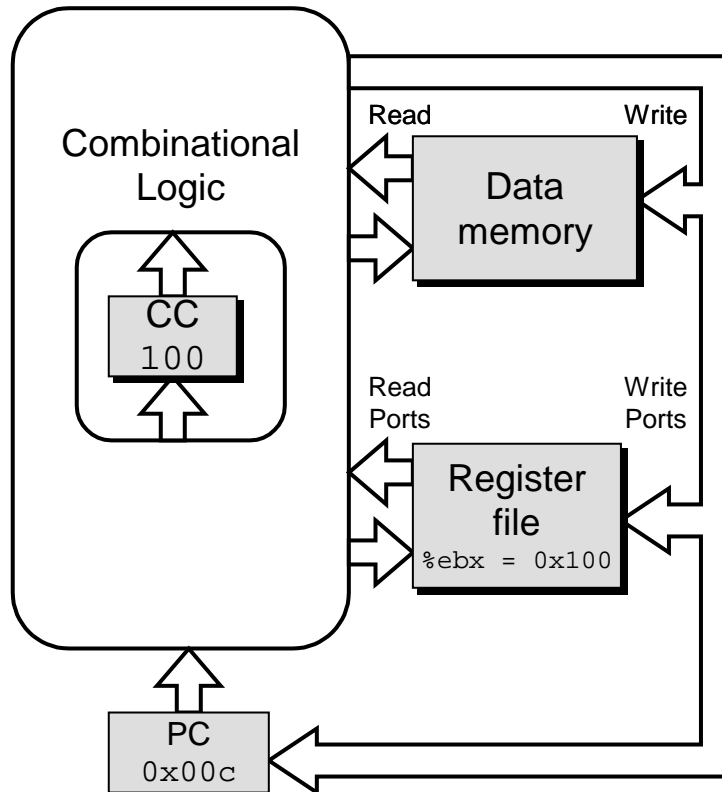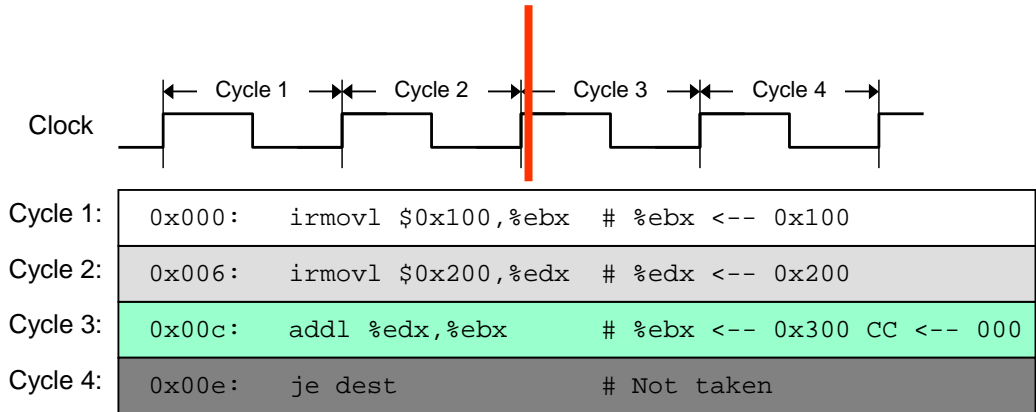



- state set according to second `irmovl` instruction
- combinational logic starting to react to state changes

SEQ Operation #3

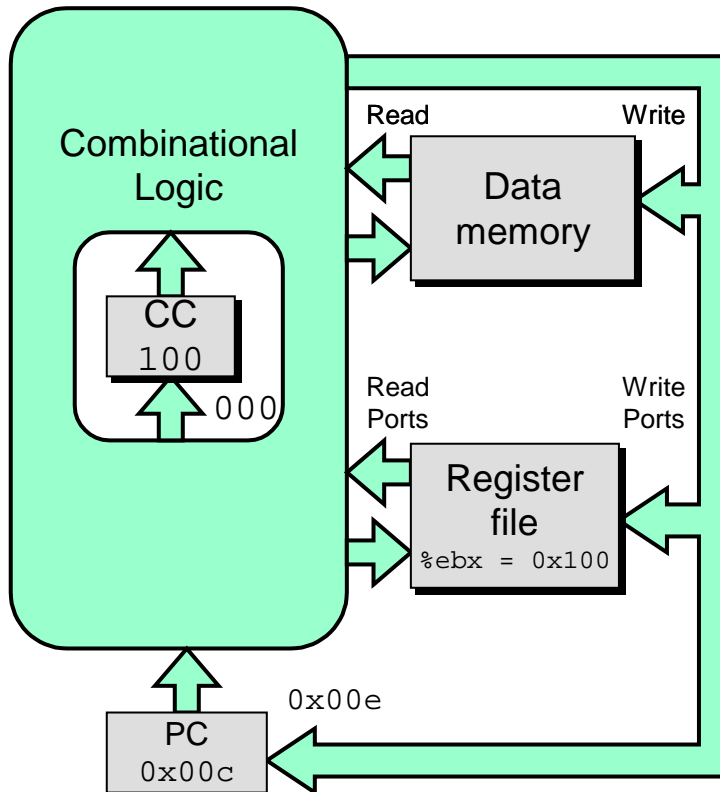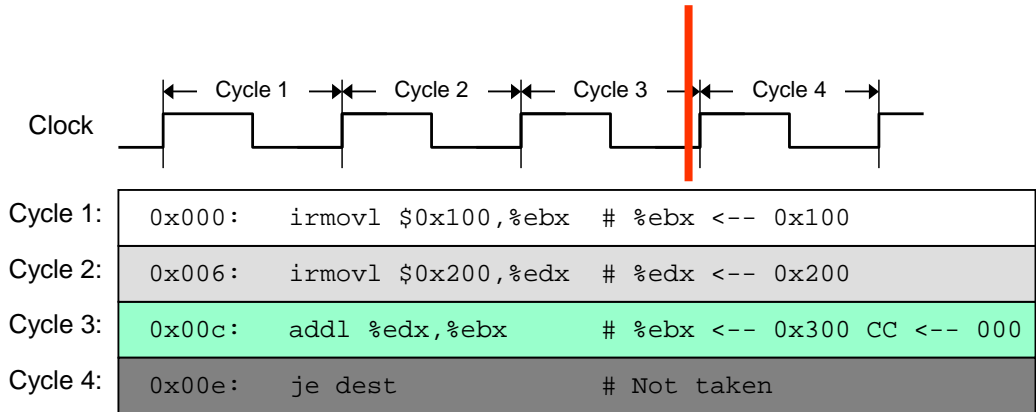



- state set according to second `irmovl` instruction
- combinational logic generates results for `addl` instruction

SEQ Operation #4

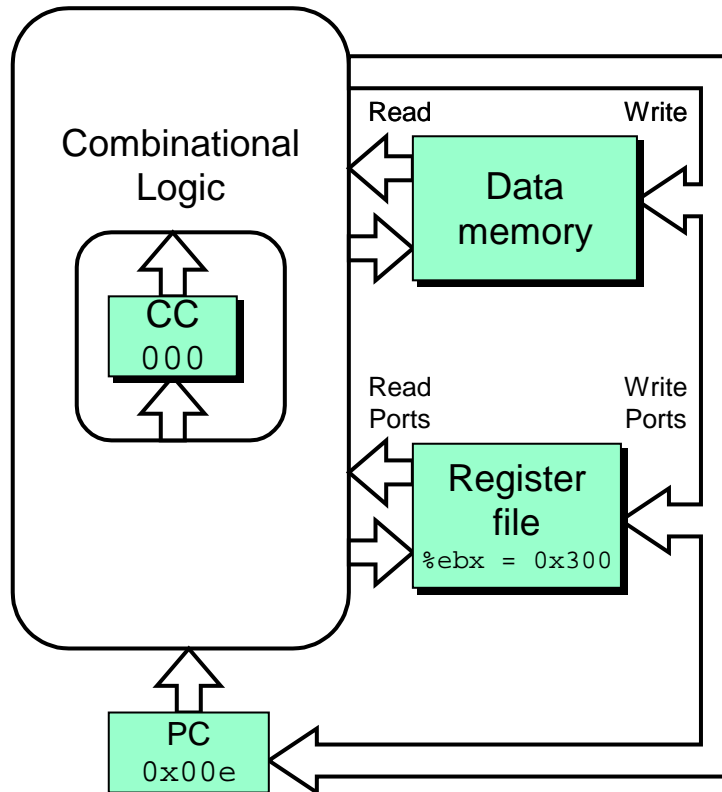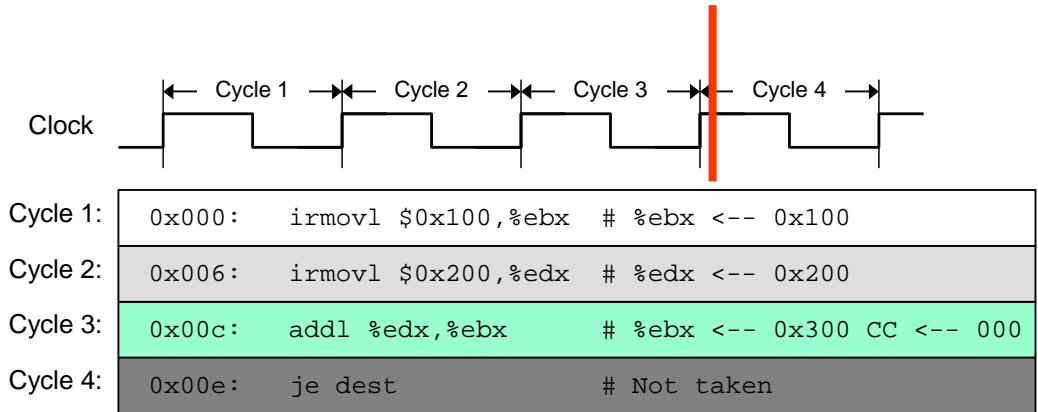

- state set according to addl instruction
- combinational logic starting to react to state changes

SEQ Operation #5

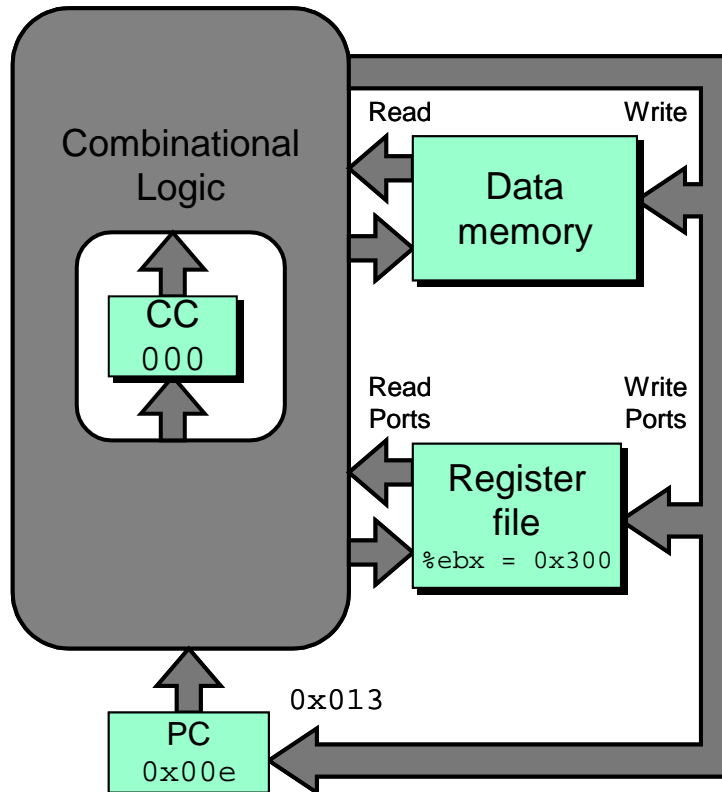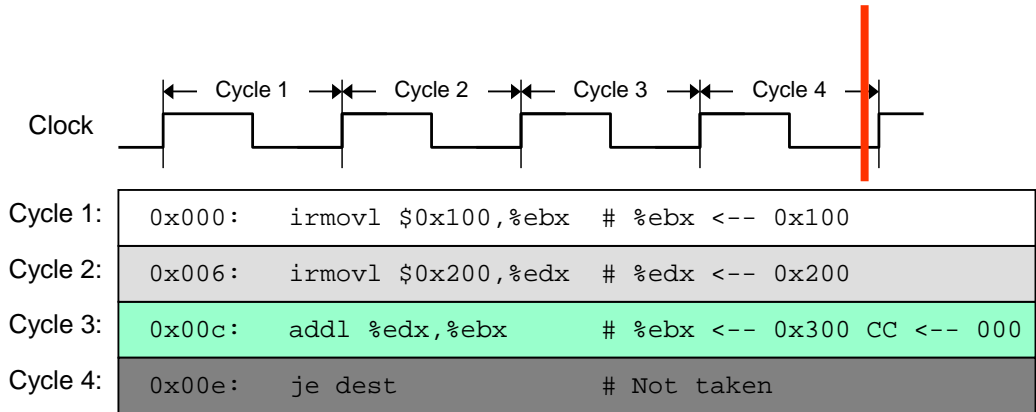

- state set according to addl instruction
- combinational logic generates results for je instruction

SEQ Summary

Implementation

- Express every instruction as series of simple steps
- Follow same general flow for each instruction type
- Assemble registers, memories, predesigned combinational blocks
- Connect with control logic

Limitations

- Too slow to be practical
- In one cycle, must propagate through instruction memory, register file, ALU, and data memory
- Would need to run clock very slowly
- Hardware units only active for fraction of clock cycle